
 


Combinational and Sequential Logic :

 

Combinational

$$\text{Output} = f(\text{Input})$$



Sequential

$$\text{Output} = f(\text{Input}, \text{Previous state})$$

Static vs Dynamic Logic Gates:


- In static logic gates

- At every point in time (except during the switching transients) each gate output is connected to either V_{DD} or V_{SS} through a low-impedance path.
- The outputs of the gates assumes at all times the value of boolean function (i.e. High or Low).

- In dynamic Logic gates

- This relies on temporary storage of signal values on the capacitance of high-impedance circuit nodes.

Static Complementary CMOS Logic :

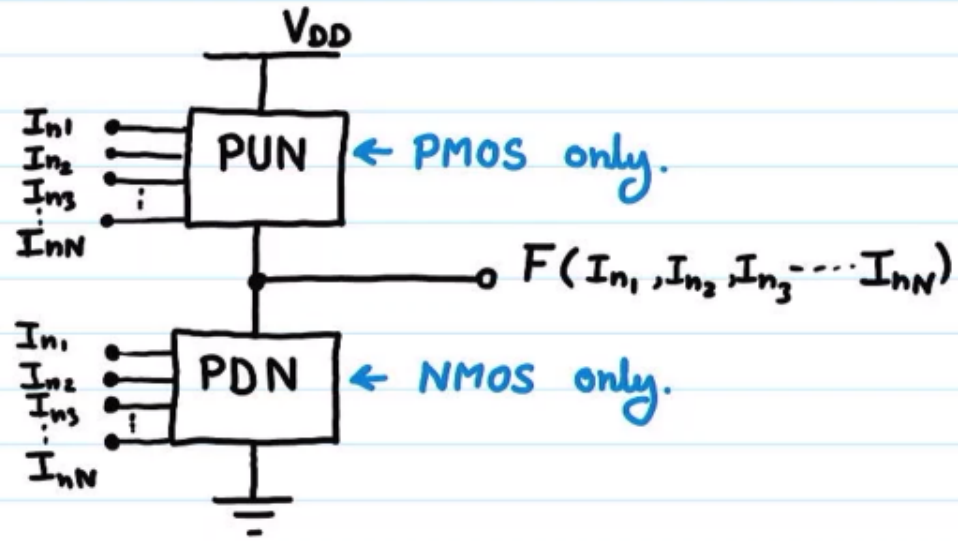

- PUN is dual of PDN.


Can be analyze using DeMorgan's Theorem.

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

PUN and PDN are dual logic network.

Example : NAND gate.

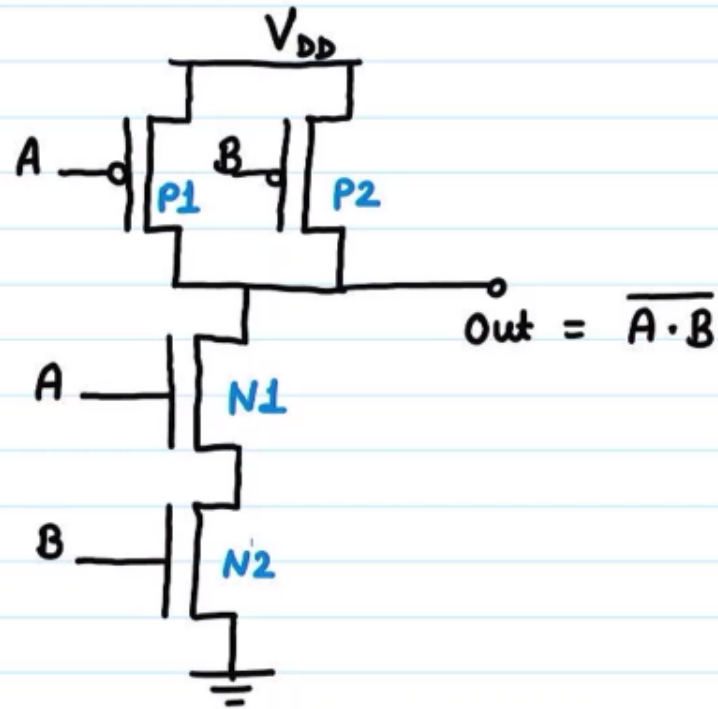

PDN : $G = A \cdot B$

PUN : $F = \bar{A} + \bar{B} = \overline{A \cdot B}$

$\overline{G(A, B)} = F(\bar{A}, \bar{B})$

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth-table of 2-INPUT NAND gate.

Static CMOS Properties :

- Full rail-to-rail swing ; High Noise Margins.
- Logic levels does not depend upon the relative device sizes ; ratioless .
- Always a path to V_{DD} or Gnd in steady-state ; low output impedance.
- Extremely high input resistance ; nearly zero steady-state input current.
- No direct path between power and ground in steady state ; no static power dissipation.
- Propagation delay is function of load capacitance and resistance of transistors.