
 


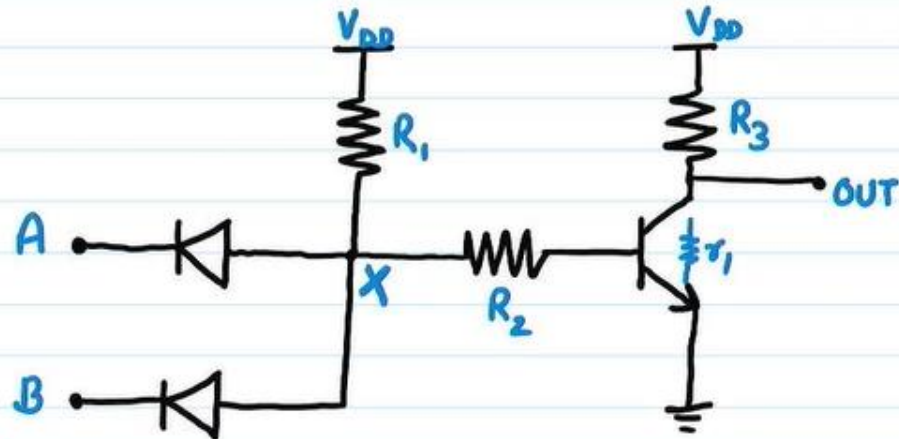TTL : Transistor - Transistor Logic uses bipolar transistors and diodes.



	A	B	OUT
→	0	0	0
→	0	1	0
→	1	0	0
→	1	1	1

AND gate




	A	B	OUT
→	0	0	1
→	0	1	1
→	1	0	1
→	1	1	0

NAND gate

$$OUT = \left(\frac{r_1}{r_1 + r_3} \right) V_{DD} \approx 0V$$

TTL : Practical Realization

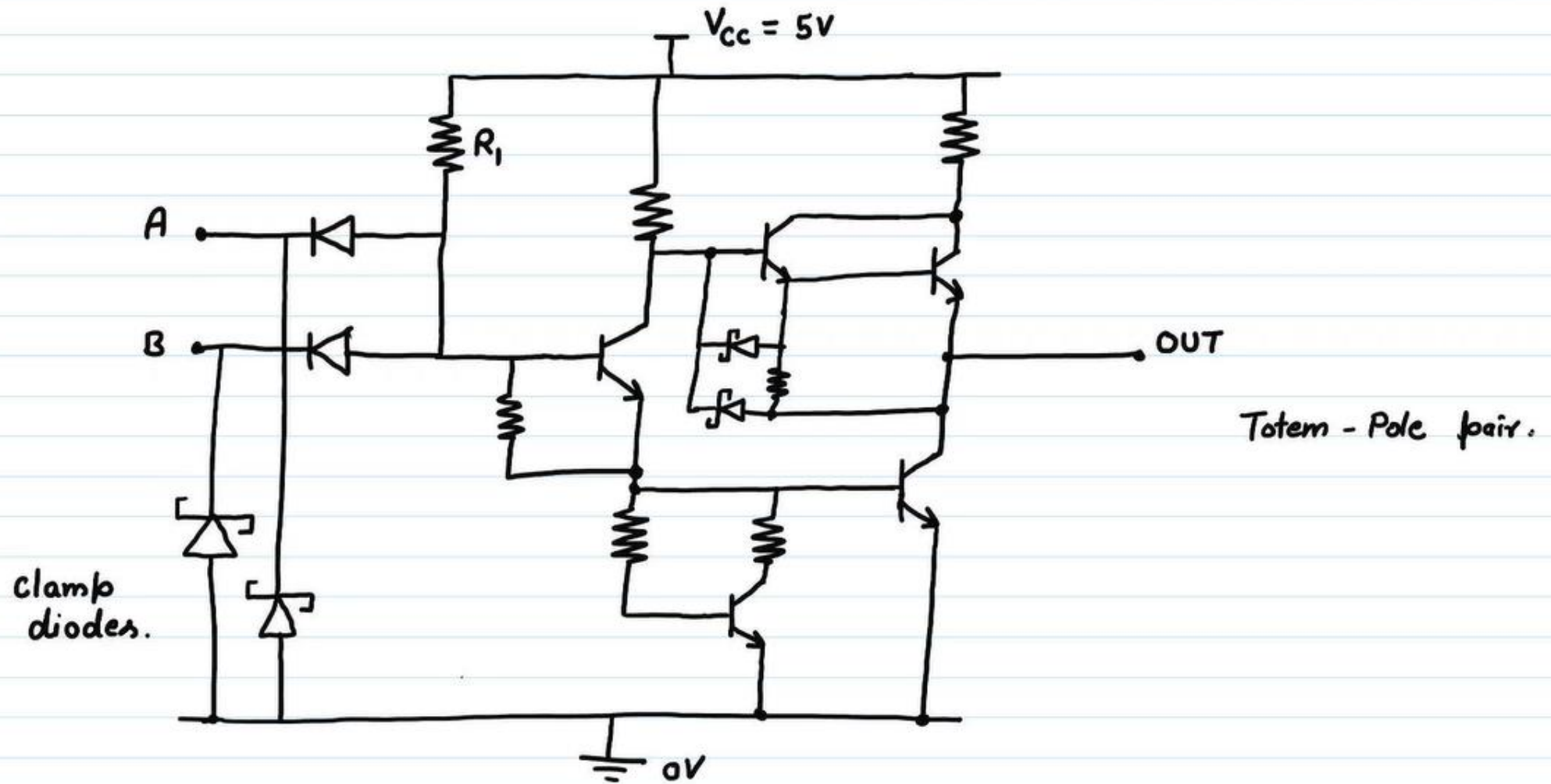

TTL vs CMOS

TTL

CMOS

Noise Margins

0.3 (high) , 0.5 (low)

0.3 V_{cc}

Input Source Currents

High in both cases.

Typically $< 1\mu A$ in both cases.

Power Consumption

Relatively High

Very Low

Output Drive Current

Asymmetric
High 0.4 - 2 mA
Low 8 - 20 mA

Symmetric
typ. 4 mA.

Power Supply

5V $\pm 10\%$

3V \rightarrow 18V



Interconnections.

Can not drive CMOS directly.



Can directly drive TTL.



CMOS / TTL Interfacing.

  


CMOS can directly
drive TTL.

  

TTL can not directly
drive CMOS.

Pull - UP resistor :

 

$R_{\text{pull-up}}$: Pull-up resistance.

if $R_{\text{pull-up}}$ is very low ($< 10\text{ k}$) : PDN of TTL increases.

if $R_{\text{pull-up}}$ is very high ($>> 10\text{ k}$) : Speed decreases.