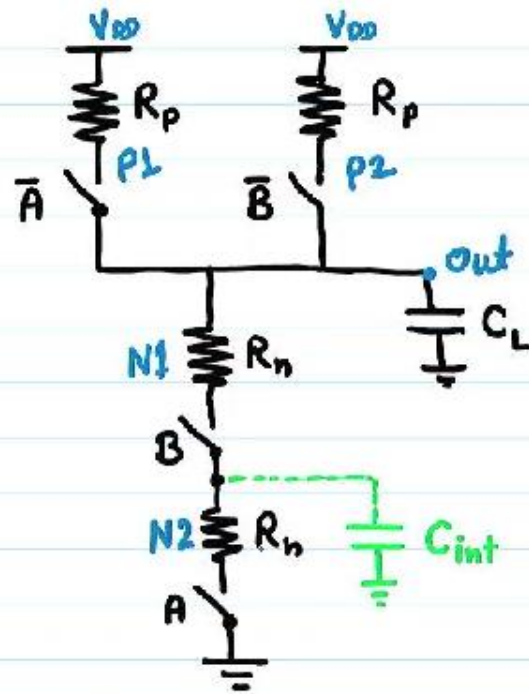


Input Pattern dependent delay :



- Delay is dependent on the patterns of input .

→ Low to High Transition

- both inputs go low

$$\text{delay is } 0.69 \cdot \frac{R_p}{2} \cdot C_L$$

- one input goes low



$$\text{delay is } 0.69 \cdot R_p \cdot C_L$$

→ High to Low Transition

- both input go high

$$\text{delay is } 0.69 \cdot 2R_n \cdot C_L$$


## Delay dependence on input pattern :

  

Input Data Pattern	Delay (psec)
$A=B=0 \rightarrow 1$	67
$A=1, B=0 \rightarrow 1$	64
$A=0 \rightarrow 1, B=1$	61
$A=B=1 \rightarrow 0$	45 <i>best case</i>
$A=1, B=1 \rightarrow 0$	80
$A=1 \rightarrow 0, B=1$	81 <i>worst case.</i>


→ NMOS =  $0.5\mu\text{m}/0.25\mu\text{m}$   
 → PMOS =  $0.75\mu\text{m}/0.25\mu\text{m}$

Transistor sizing of complex CMOS gates:

 

$$OUT = \overline{D + A \cdot (B + C)}$$

## Fan - In of Gate :

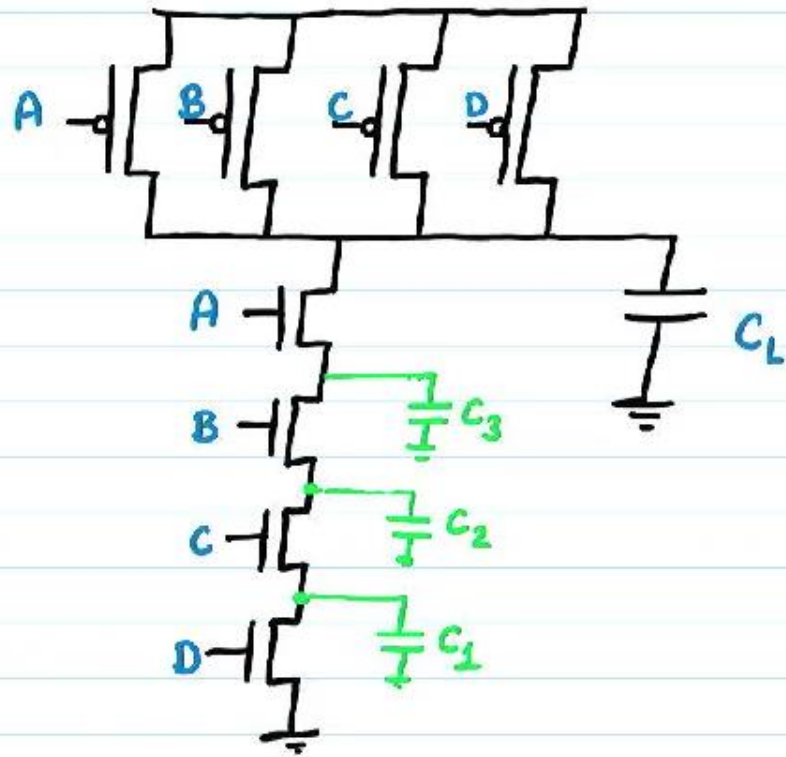


Distributed RC model  
(Elmore delay)

$$t_{pHL} = 0.69 \cdot R_{eqn} (C_1 + 2C_2 + 3C_3 + 4C_L)$$

Propagation delay degrades rapidly as a function of fan-in. - Quadratically in the worst case.

## Design Techniques for fast logic gates.

- Progressive Sizing :

 

Distributed RC line

$$M_1 > M_2 > M_3 > \dots > M_N$$

(the transistor closest to the output is smallest)

Can reduce delay by more than 20%.