
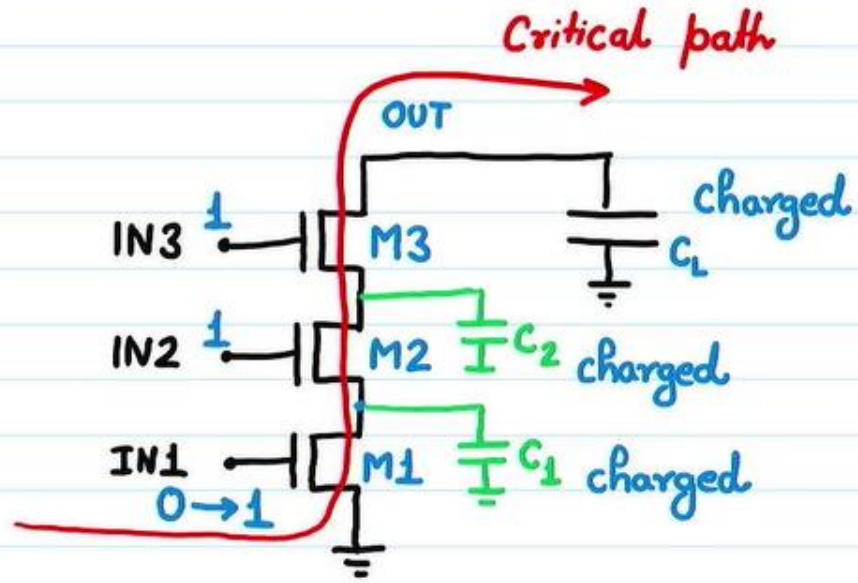

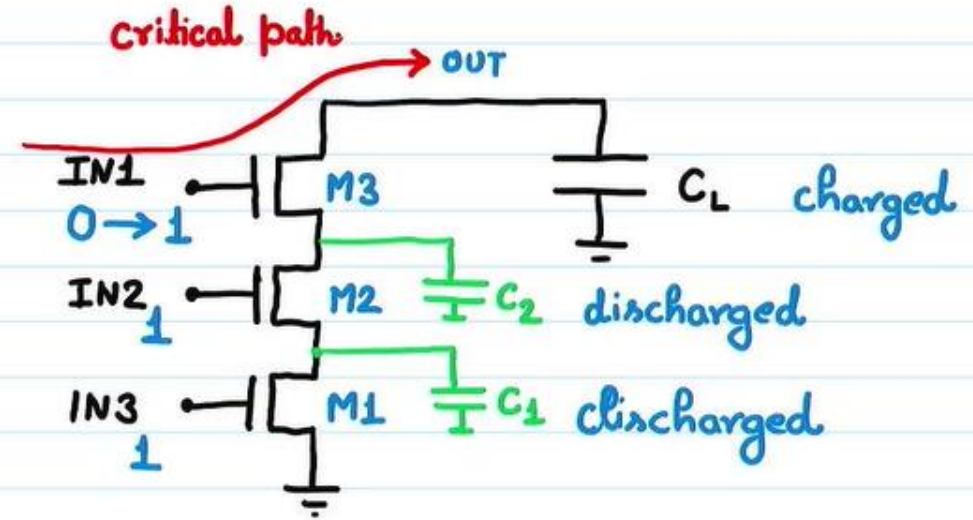
## Design Techniques 2 for fast CMOS gates :



Overall delay is determined by time to discharge  $C_1$ ,  $C_2$  and  $C_L$ .




Overall delay is determined by time to discharge only  $C_L$ .


## Design techniques 3 for CMOS gates :

- Find alternate logic structures to reduce overall delay.

$$F = ABCDEFGH$$


 

 
$$\begin{aligned}\text{overall delay} &= 2 + 2 + 2 + 1 \\ &= 7 \text{ ps.}\end{aligned}$$



$$\text{overall delay} = 10 + 1 = 11 \text{ ps.}$$

## Dynamic Logic Gates :

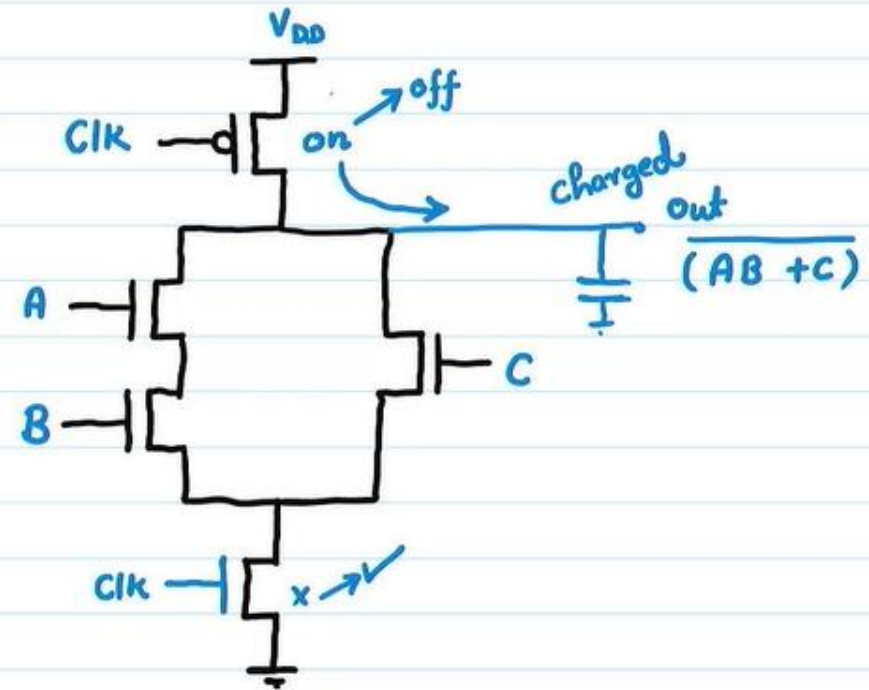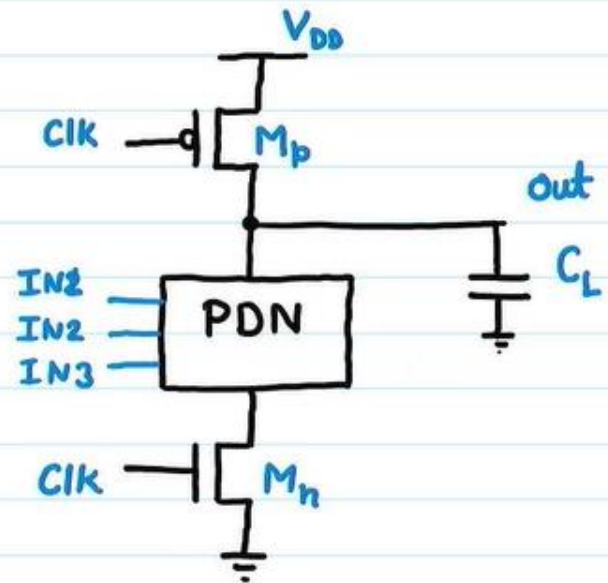

Two phase operation

Precharge ( $CLK = 0$ )

Evaluate ( $CLK = 1$ )



## Properties of Dynamic gates :

- Logic function is implemented by PDN only.
  - No. of transistors needed is  $N+2$  ( $2N$  in case of static gates)
- Full rail-to-rail output.
- Ratioless design - sizing of device does not affect the logic level.
- Faster switching speed
  - 1) reduced load capacitance due to lower input capacitance.
  - 2) reduced load capacitance due to smaller output loading.
  - 3)  $I_{sc}$  . all the current by PDN goes into discharging  $C_L$ .



## Properties Continued ...

- Overall power dissipation usually higher than static CMOS.
  - Higher transition probabilities.
  - Extra load on clk.
- Needs a pre-charge / evaluate clock.