
Used to add signals generated by various

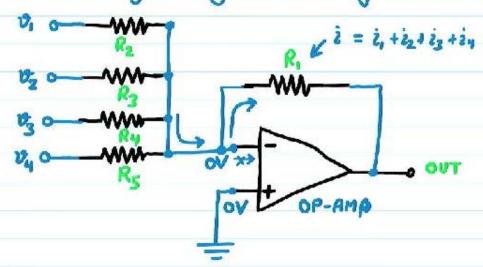

$$\dot{z}_1 = \frac{v_1 - o}{R_2} = \frac{v_1}{R_2}$$

$$\dot{z}_2 = \frac{v_2}{R_3} , \quad \dot{z}_3 = \frac{v_3}{R_4} , \quad \dot{z}_4 = \frac{v_4}{R_3}$$

$$v_0 = -R_1 \left[\frac{v_1}{R_2} + \frac{v_2}{R_3} + \frac{v_3}{R_4} + \frac{v_4}{R_5} \right]$$

$$v_o = -\left[v_1 + v_2 + v_3 + v_4\right]$$



