

4) Module Level Design Stage :

- Design and simulate functional module using HDL.
- Auto-generation of layout for the complete module using synthesis.

```
module full-adder (in-x, in-y, carry-in, sum-out, carry-out);
```

```
    input in-x;
```

```
    input in-y;
```

```
    input carry-in;
```

```
    output sum-out;
```

```
    output carry-out;
```


```
    wire w-sum1;
```

```
    wire w-carry1;
```

```
    wire w-carry2;
```

```
    assign carry-out = w-carry1 | w-carry2;
```
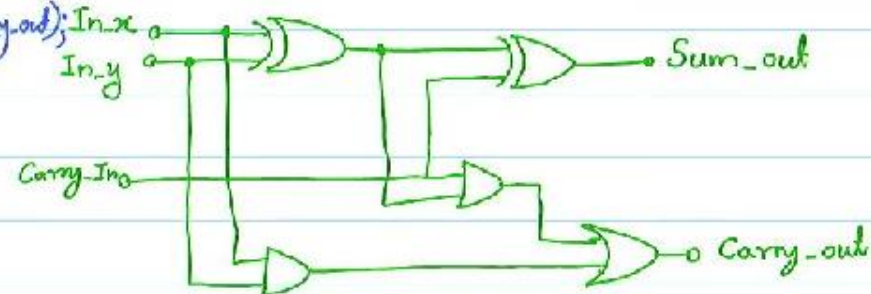
```
    // instantiate two half-adder to make the circuit
```



```
half-adder u1_half-adder
```



```
(
    .in-x (in-x),
    .in-y (in-y),
    .out-sum (w-sum1),
    .out-carry (w-carry1),
);
```

```
half-adder u2_half-adder
```

```
(
    .in-x (w-sum1),
    .in-y (carry-in),
    .out-sum (sum-out),
    .out-carry (w-carry2),
);
```

```
endmodule
```

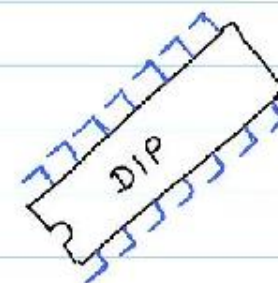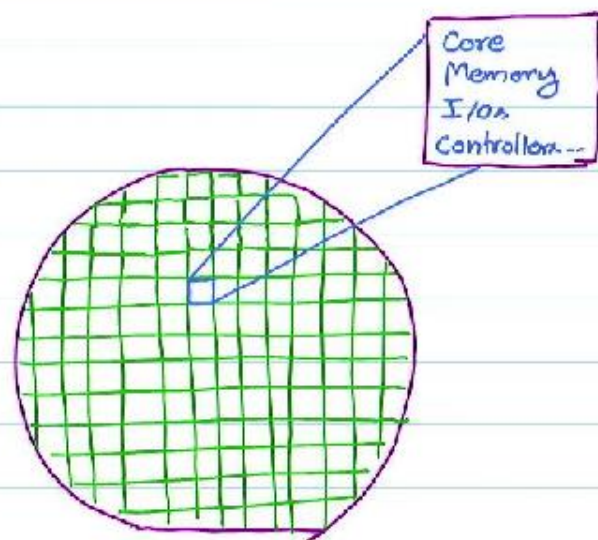- 5) IC Design Stage :
- Complete function design (various Analog and Digital Modules)
 - Timing and power constraints taken from circuit design stage.
 - Synthesize complete function using HDL.
 - Place and route for minimum space / power density.



Package.

6) System Design stage :

- Processor
- RFIC
- RF Switches
- Memory
- Screen driver.

- Printed circuit Board (PCB)

☐ Multiple ICs are used to make complete product.

☐ For example:

- Processor.
- RFIC.
- RF Switches.

iSuppli Google Nexus One Teardown Analysis
Exploded View



Copyright © 2010 iSuppli Corporation



Basic Circuit Elements :

- Resistor (ohm's law)
- Capacitor (based on energy storage in electric field)
- Inductor (based on energy storage in magnetic field)
- Voltage Sources (like battery)
- Current Sources (constant current)

1) Resistor (R)

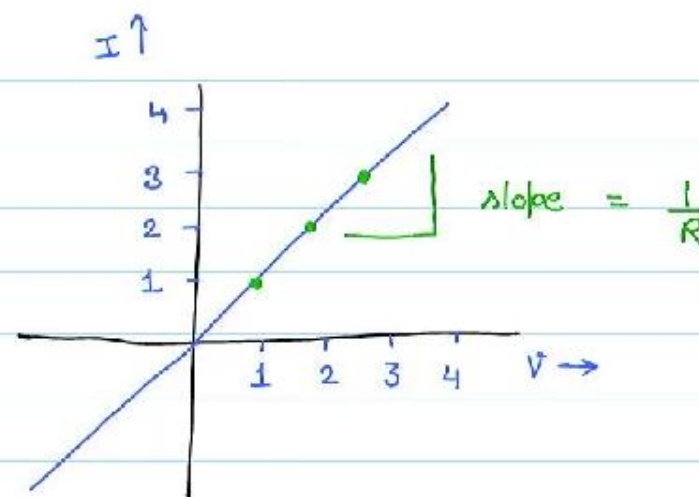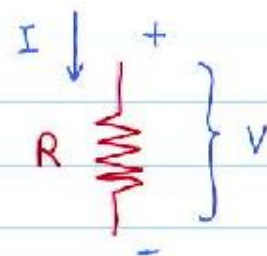

- All wires and circuit connections have resistance


↳ Though we most often approximate them to "0".

2) Capacitor (c) :


Any two conductors a and b, separated by an insulator.



symbol

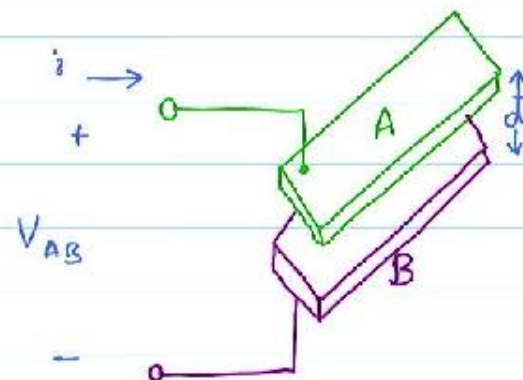

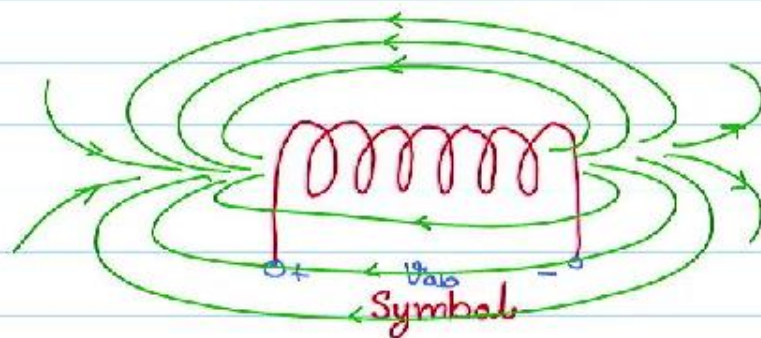3) Inductor : Inductors are the dual of capacitors - they store the energy in magnetic fields.



Capacitor

$$i = C \frac{dV}{dt}$$

$$E = \frac{1}{2} C V^2$$

Inductor

$$v = L \frac{di}{dt}$$

$$E = \frac{1}{2} L I^2$$