

- System specifications are behavioral in nature.
- Handling of large complex designs is possible through CAD softwares.
- Impractical to use SPICE for simulating large digital circuits
 - Time complexity.
- Manual optimization of design Boolean expressions are difficult.


Verilog

- Has good acceptance in ASIC.
- Good for low-level designs
 - RTL and below
- Fast simulations
- Relatively simple (similar to C lang.)
- Popular in N. America, Asia and Japan.

VHDL

- Relatively weak in low-level design.
- Superior in system level design.
- Slower simulations.
- Relatively complex.
- Popular in Europe.

Top-down Design Approach :

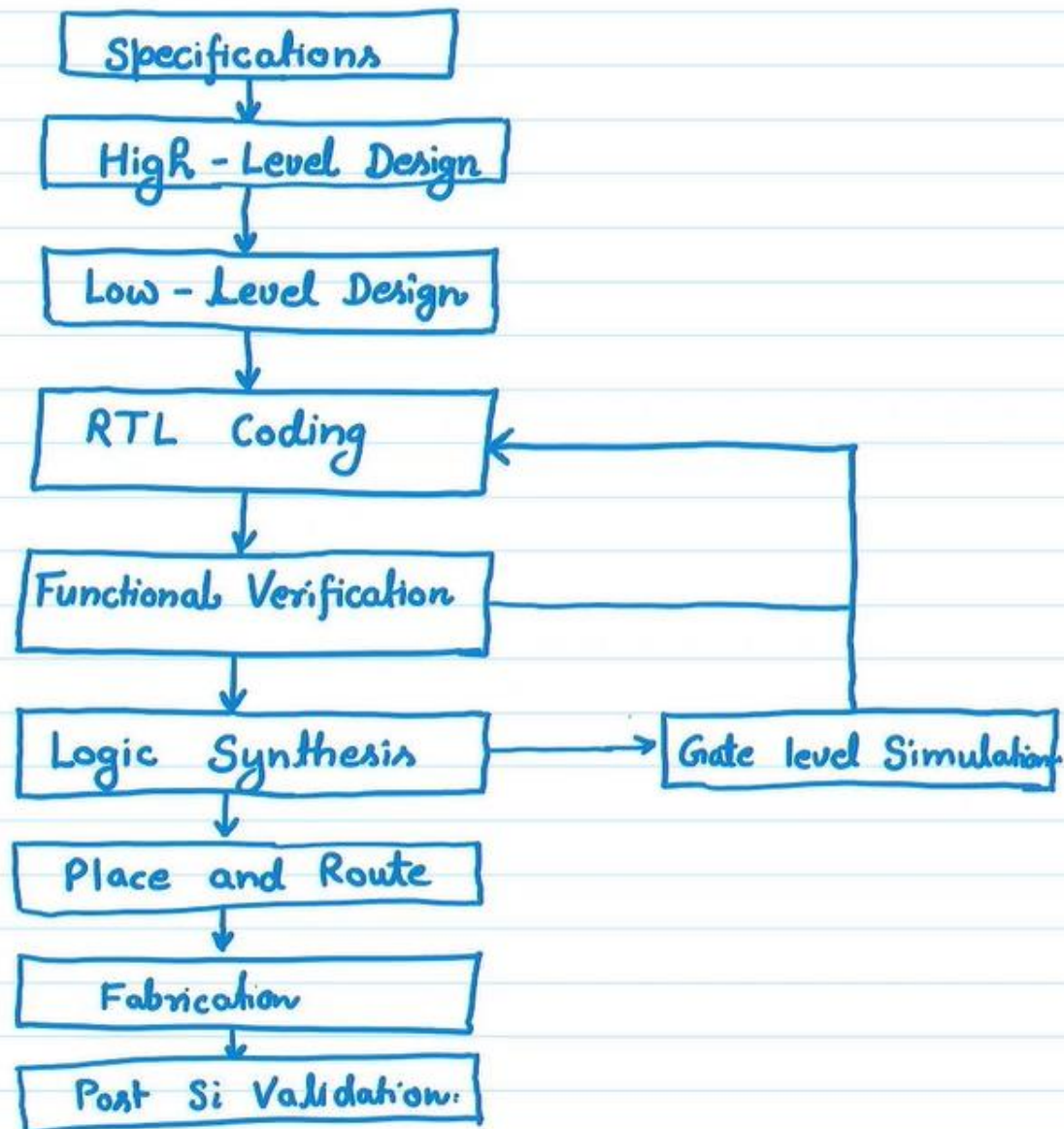

Definition of Module in Verilog :

module module_name (port_list)

port declaration

' include directives

variable declarations

assignments

lower-level module instantiation.

initial and always blocks.

tasks and functions.

} body

endmodule

Comments in Verilog


- One line comment

// -----

- Block comments

/* ----- */

Coding Style : Structural

 


```
module mux_4_to_1 (Out, In0, In1, In2, In3, Sel1, Sel0);  
  output Out;  
  input In0, In1, In2, In3, Sel0, Sel1;  
  
  wire NotSel0, NotSel1;  
  wire Y0, Y1, Y2, Y3;  
  
  not (NotSel0, Sel0);  
  not (NotSel1, Sel1);  
  and (Y0, In0, NotSel1, NotSel0);  
  and (Y1, In1, NotSel1, Sel0);  
  and (Y2, In2, Sel1, NotSel0);  
  and (Y3, In3, Sel1, Sel0);  
  or (Out, Y0, Y1, Y2, Y3);  
  
endmodule
```

- Circuit is specified in terms of lower-level components (NAND, NOR etc.). These are connected with internal signals.

Synthesis is easy.


Coding Style : Data Flow

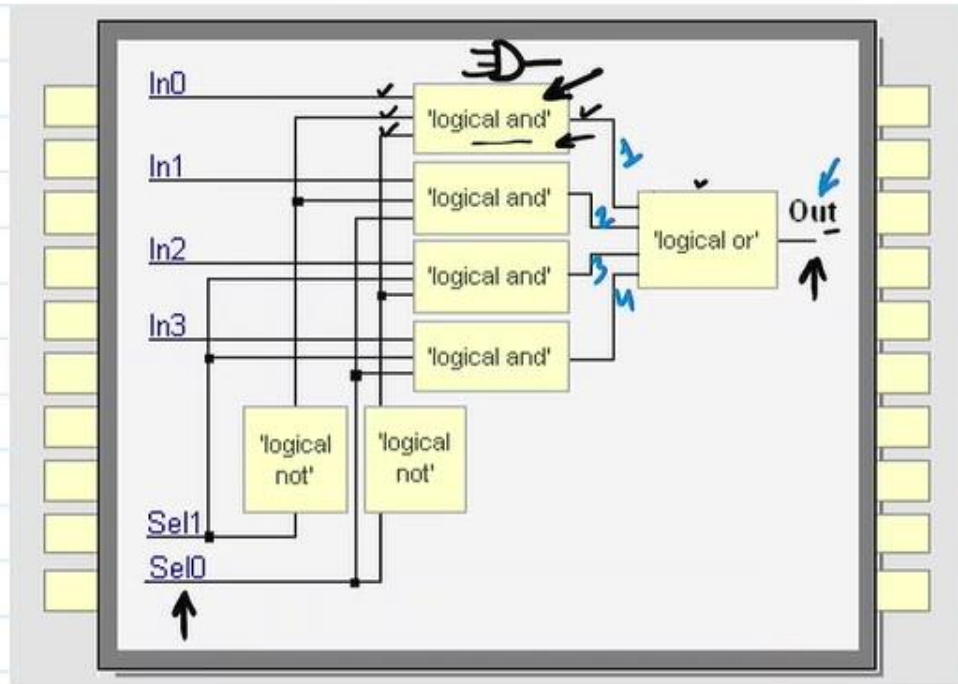

```
module mux_4_to_1 (Out, In0, In1, In2, In3, Sel1, Sel0);  
    output Out;  
    input In0, In1, In2, In3, Sel0, Sel1;  
    assign Out = (~Sel1 & ~Sel0 & In0) | (~Sel1 & Sel0 & In1) |  
                (Sel1 & ~Sel0 & In2) | (Sel1 & Sel0 & In3);  
endmodule
```

- Similar to logical equations,
- Expressions are assigned to output.
- Synthesis is okay.

Coding Style : Behavioral

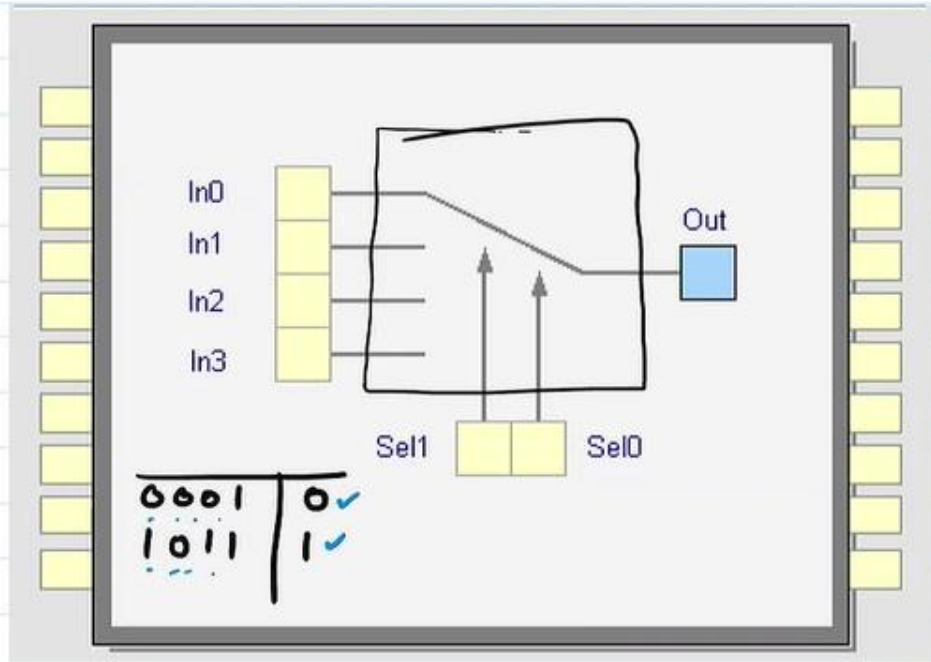

```
module mux_4_to_1 (Out, In0, In1, In2, In3, Sel1, Sel0);  
  output Out;  
  input In0, In1, In2, In3, Sel0, Sel1;  
  reg Out;  
  
  always @ (Sel1 or Sel0 or In0 or In1 or In2 or In3)  
  begin  
    case ((Sel1, Sel0))  
      2'b00 : Out = In0;  
      2'b01 : Out = In1;  
      2'b10 : Out = In2;  
      2'b11 : Out = In3;  
      default : Out = 1'bx;  
    endcase  
  end  
  
endmodule
```

- Specify the circuit in terms of its expected behavior.
- close to natural language description.
- Most difficult to synthesize.