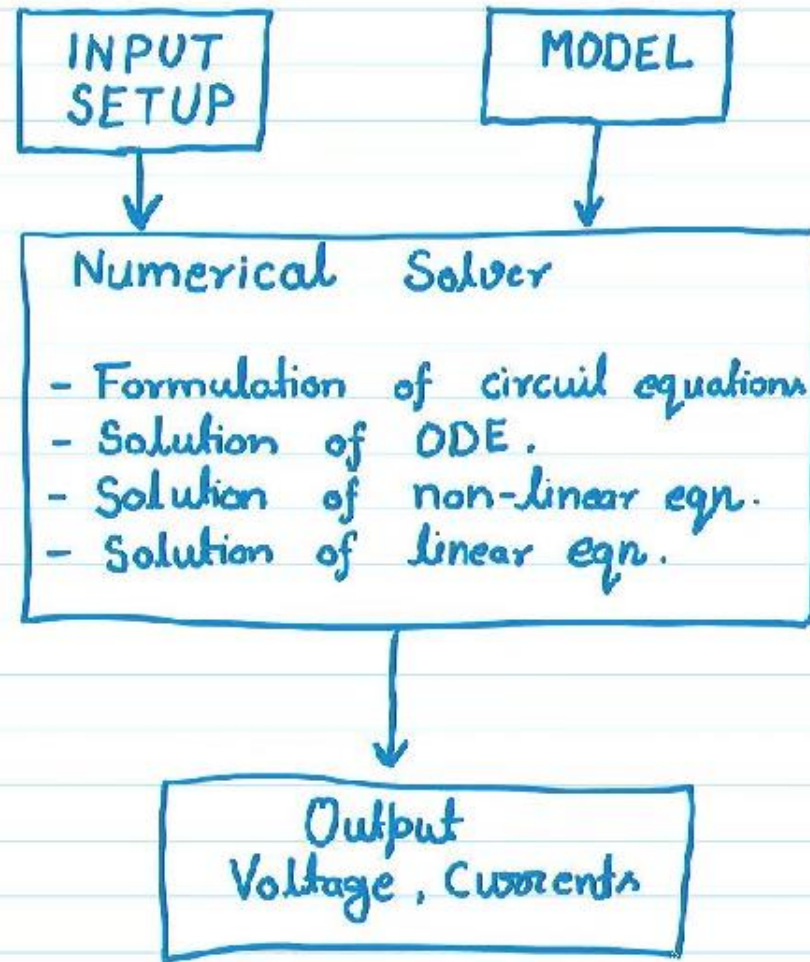


Circuit Simulation :

To exit full screen, press Esc



Circuit Analysis :

To exit full screen, press Esc

- Electrical circuit elements are idealized models of physical devices that are defined by relationships between their terminal voltages and currents.
- An electrical circuit is a connection of circuit elements into one or more closed loops
- Basic quantities are voltage, currents and power.
- Circuit elements can be active or passive.
- The "Sign Convention" is important in computing output.

Kirchhoff's Current Law (KCL) :


KCL states that the algebraic sum of currents entering a node (or a closed boundary) is zero.

- Before applying KCL, sign convention is very important.

Current entering the node " - "

Current leaving the node " + "

- Applying KCL to circuit :

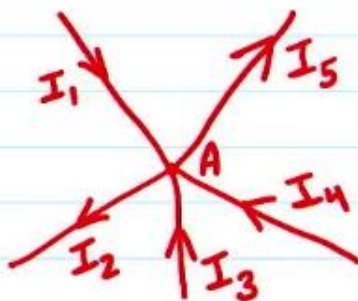

$$-I_1 + I_2 - I_3 - I_4 + I_5 = 0$$

$$I_2 + I_5 = I_1 + I_3 + I_4$$


$$\sum_{n=1}^N I_n = 0$$

Kirchhoff's Voltage Law (KVL)

To exit full screen, press Esc

- KVL states that the algebraic sum of all voltages around a closed path (or loop) is zero.

For example:

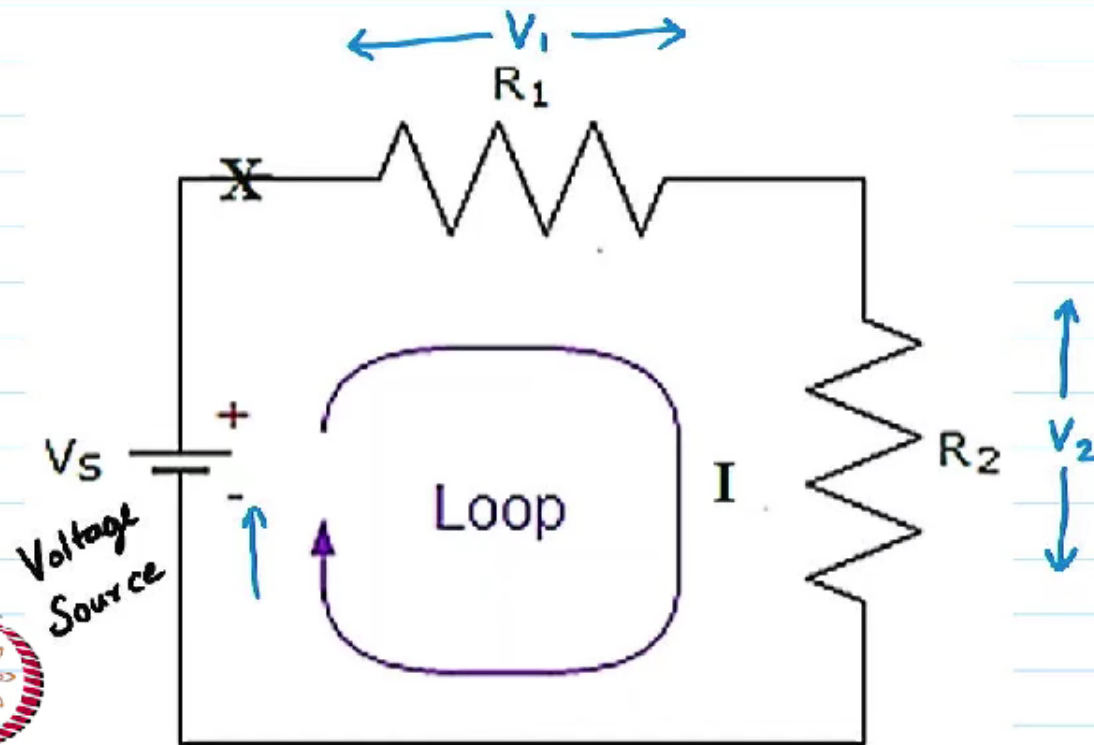

$$IR_1 + IR_2 - V_s = 0$$

$$\sum_{n=1}^N V_n = 0$$

Why need KVL and KCL?

- Ohm's law by itself is not sufficient to analyze circuits.
- Coupled with KCL and KVL to solve the circuits.
- KCL is based upon the law of conservation of charge.
- KVL is based upon the law of conservation of energy.
- KVL and KCL can be applied to AC circuits as well, provided we use phasor sums instead of algebraic sums.

How do we solve circuits?

To exit full screen, press Esc

MESH Analysis

- Loop : It is a closed path with no node passed more than once.
- Mesh : A mesh is a loop that does not contain any other loop within it.
- Mesh Analysis : is applicable to circuits that are ~~linear~~ planar.
- Planar Circuits : A planar circuit is one that can be drawn in a plane with no branch crossing one another.
- Non-planar circuits : A non-planar circuit is one that can be drawn in a plane with branches crossing one another.

Example :

Apply KVL in mesh 1.

$$-V_1 + i_1 R_1 + i_3 R_3 = 0 \quad \text{--- (1)}$$

Apply KCL at node b

$$\begin{aligned} -i_1 + i_2 + i_3 &= 0 \\ i_3 &= i_1 - i_2 \end{aligned} \quad \text{--- (2)}$$

putting i_3 in eqn. 1,


$$V_1 = (R_1 + R_3) i_1 - R_3 i_2$$

Apply KVL in mesh 2.

$$R_2 i_2 + V_2 - R_3 i_3 = 0$$

$$R_2 i_2 + V_2 - R_3 (i_1 - i_2) = 0$$


$$V_2 = -R_3 i_1 + (R_1 + R_2) i_2$$

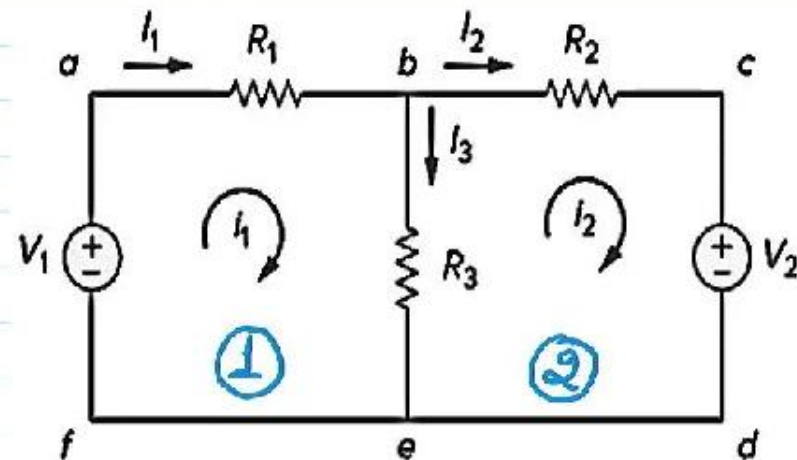

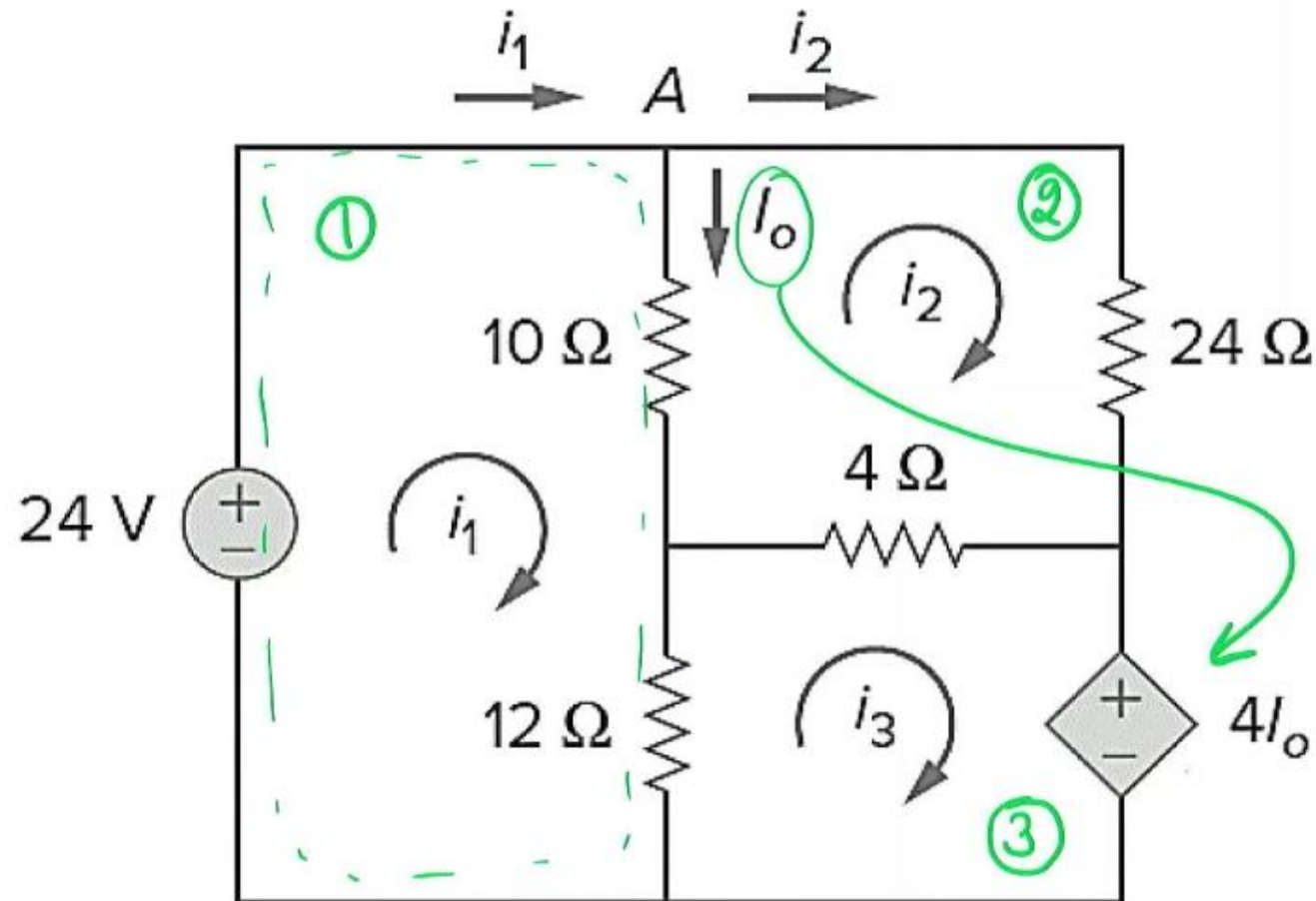Example:

To exit full screen, press Esc

Find mesh currents i_1 , i_2 , i_3 and i_o using mesh analysis.



Example:

Applying KVL in mesh 1.


$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0 \Rightarrow 11i_1 - 5i_2 - 6i_3 = 12 \quad (1)$$

Applying KVL in mesh 2, ✓

$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0 \Rightarrow -5i_1 + 19i_2 - 2i_3 = 0 \quad (2)$$

Applying KVL in mesh 3
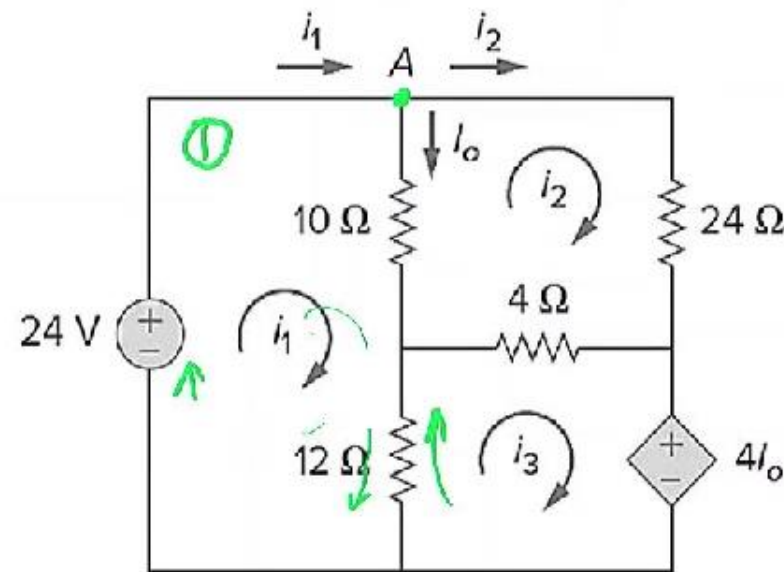
$$4I_o + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$



Example:

But at node A, $I_o = i_1 - i_2$, so that

$$\Rightarrow 4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$\Rightarrow -i_1 - i_2 + 2i_3 = 0 \quad (3)$$

Using Cramer's rule to solve 3 unknown variables and writing in matrix form.

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \det \begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} = 192$$

$$\Delta_1 = \det \begin{bmatrix} 12 & -5 & -6 \\ 0 & 19 & -2 \\ 0 & -1 & 2 \end{bmatrix} = 432$$

$$\Delta_2 = \det \begin{bmatrix} 11 & 12 & -6 \\ -5 & 0 & -2 \\ -1 & 0 & 2 \end{bmatrix} = 144$$

$$\Delta_3 = \det \begin{bmatrix} 11 & -5 & 12 \\ -5 & 19 & 0 \\ -1 & -1 & 0 \end{bmatrix} = 288$$

$$i_1 = \frac{\Delta_1}{\Delta} = 2.25 A, i_2 = \frac{\Delta_2}{\Delta} = 0.75 A$$
$$i_3 = \frac{\Delta_3}{\Delta} = 1.5 A$$