

- Various techniques, all based upon Kirchhoff's law, are used for the circuit analysis.
- The main techniques are:
 - Superposition Theorem
 - Thevenin's Theorem
 - Norton's Theorem
 - Maximum Power Transfer Theorem
- Each of these techniques have strengths aimed at solving particular types of circuit problem.

- Superposition Theorem ;

→ It helps us to analyze a linear circuit with more than one independent sources.


→ The output of a circuit is determined by summing the individual responses of each independent sources.

→ The idea of superposition rests on the linearity property.


→ It is the property of an element describing a linear relationship between cause and effect.

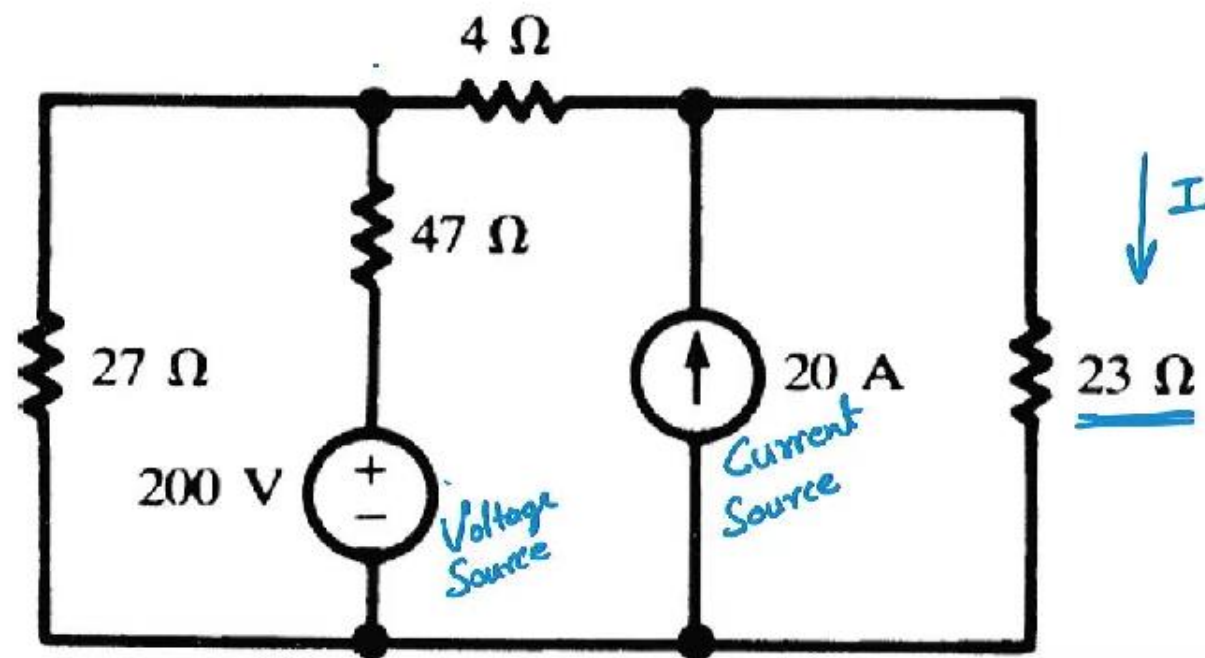Example :

Calculate the current in $23\ \Omega$ resistor.



Current Divider Rule "CDR" Calculator

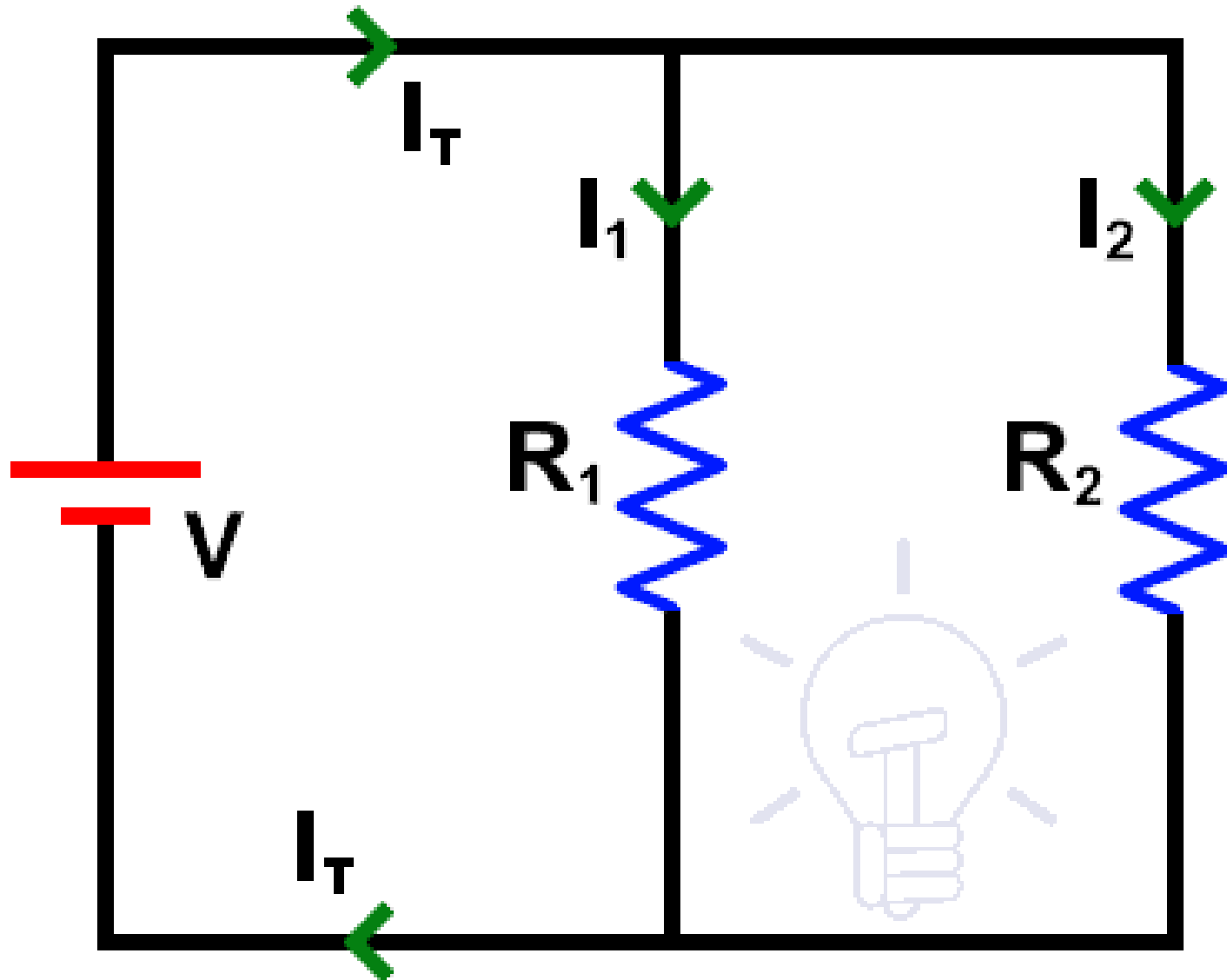

$$I_1 = I_T \frac{R_2}{R_1 + R_2}$$

WWW.ELECTRICALTECHNOLOGY.ON

$$I_2 = I_T \frac{R_1}{R_1 + R_2}$$


Step. 1: Take Voltage source

To exit full screen, press Esc

$$R_{eq} = 47 + \frac{(27)(4+23)}{27+4+23} = 60.5 \Omega$$

$$I_T = \frac{200}{60.5} = 3.31 \text{ Amp}$$
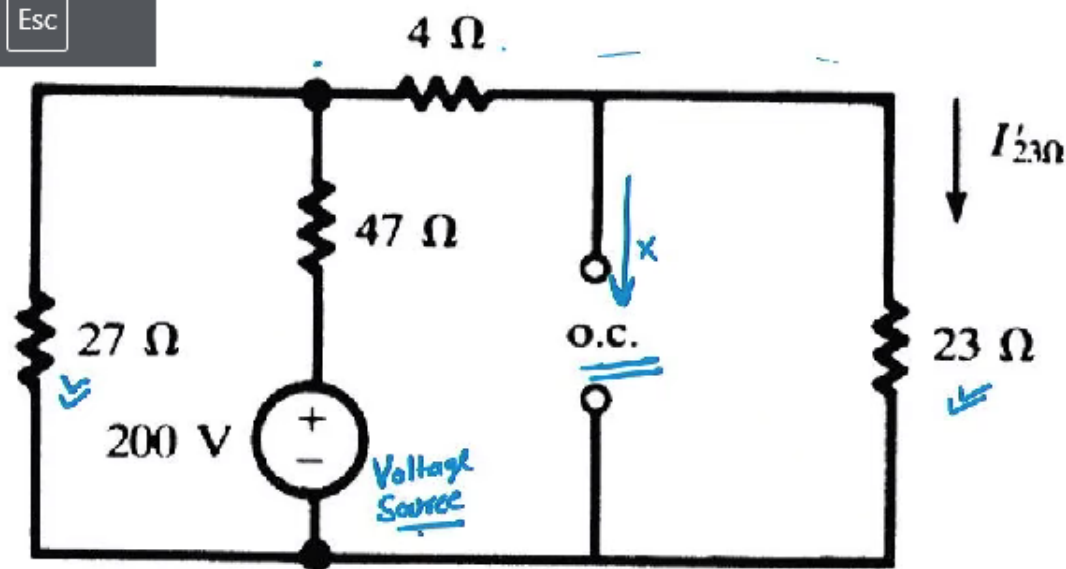
$$I'_{23\Omega} = \left(\frac{27}{54}\right) \times 3.31$$
$$= 1.65 \text{ Amp.}$$



Step. 1: Take Voltage source

$$R_{eq} = 47 + \frac{(27)(4+23)}{27+4+23} = 60.5 \Omega$$

$$I_T = \frac{200}{60.5} = 3.31 \text{ Amp}$$

$$I'_{23\Omega} = \left(\frac{27}{54} \right) \times 3.31$$

$$= 1.65 \text{ Amp.}$$

Step. 2: Take only current source:



$$R_{eq} = 4 + \frac{(27)(47)}{27+47} = 21.15 \Omega$$

$$I''_{23\Omega} = \left(\frac{21.15}{21.15 + 23} \right) (20) = 9.58 \text{ Amp}$$

So, Total Current

$$I_{23\Omega} = 1.65 + 9.58$$

$$= 11.23 \text{ Amp.}$$

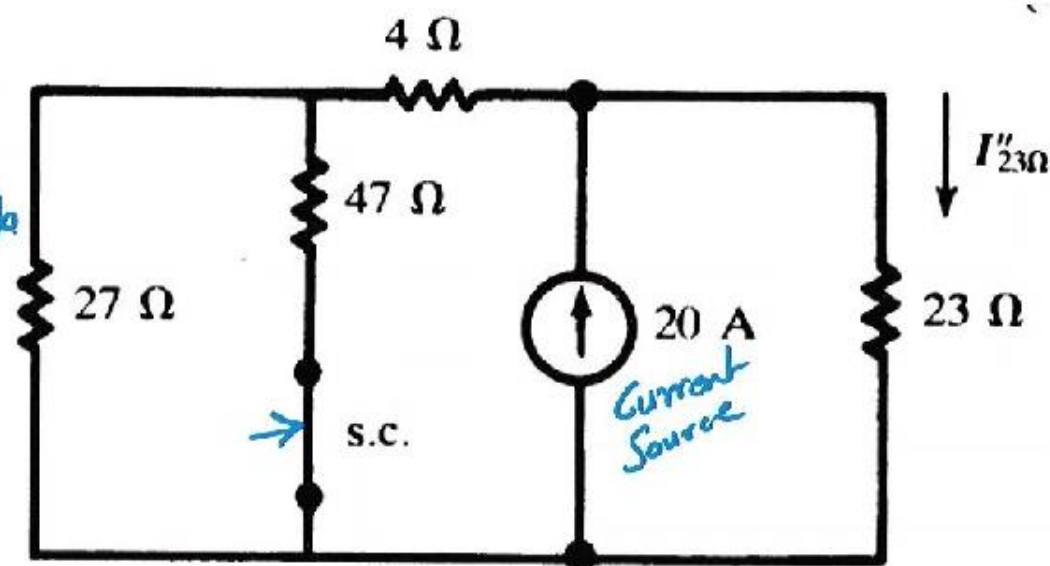
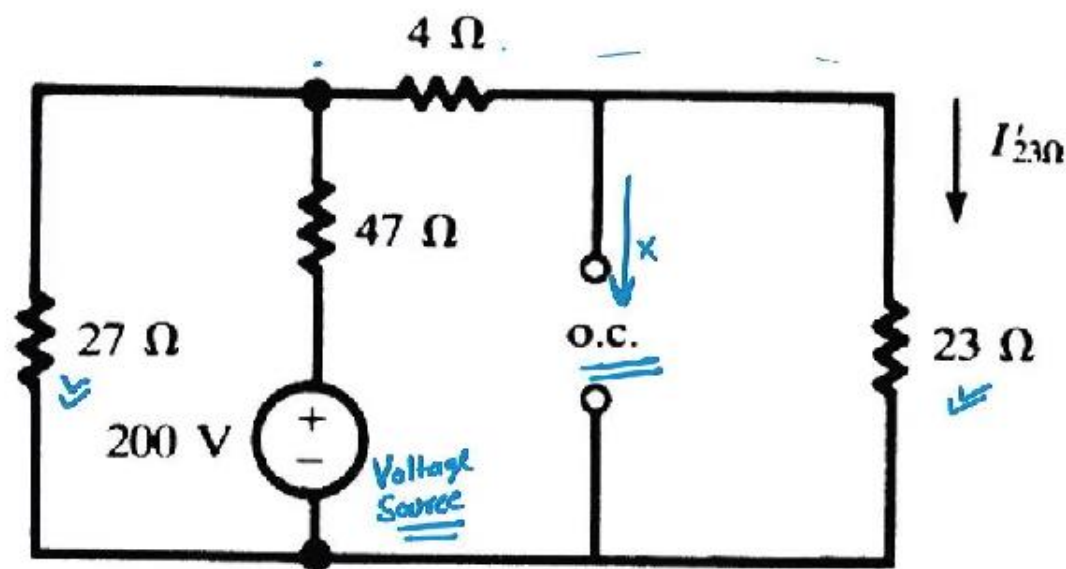


Thevenin's Theorem :

Thevenin theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{TH} in series with a resistor R_{TH} , where V_{TH} is the open circuit voltage at the terminals and R_{TH} is the input or equivalent resistance at the terminals when the independent sources are turned off.

→ It is useful in the circuit analysis of power or battery systems where it will have effects on the adjoining part of the circuit.

Example :

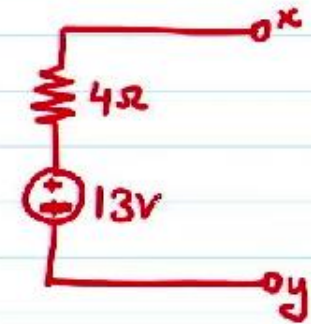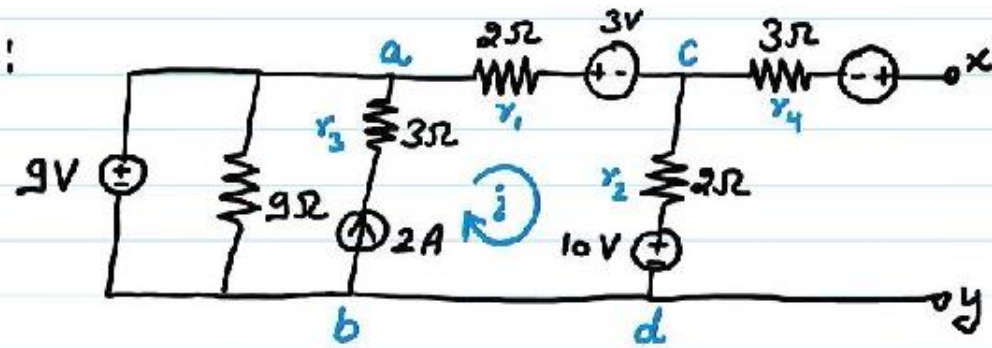

Solution: Apply KVL at loop acdb

$$\begin{aligned}
 -V_{ab} + i r_1 + 3 + i r_2 + 10 &= 0 & [V_{a-b} = 9V] \\
 -9 + 2i + 3 + 2i + 10 &= 0 \\
 4i &= -4 \Rightarrow i = -1 A
 \end{aligned}$$

$$\begin{aligned}
 \text{Drop in } r_2 &\Rightarrow 2 \times (-1) = -2V \\
 V_{c-d} &= 10 - 2 = 8V \\
 \underline{V_{oc}} &= V_{c-d} + 5 = \underline{13V}
 \end{aligned}$$

To find R_{TH} ,

$$R_{TH} = 3 + \frac{2 \times 2}{2+2}$$


$$\underline{R_{TH}} = \underline{4\Omega}$$

Norton's Theorem :

Norton theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source I_N , in parallel with a resistor R_N ,

where I_N is the short-circuit current through the terminals,
 R_N is the input or equivalent resistance at the terminals when independent ∇ sources are turned off.


Example :

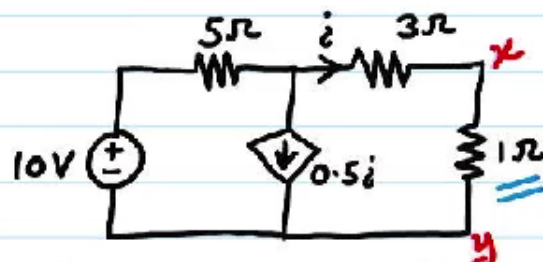

Find the current in 1Ω resistor.

Solution: Remove 1Ω , $V_{oc} = 10V$

Next, short circuit the output terminal.

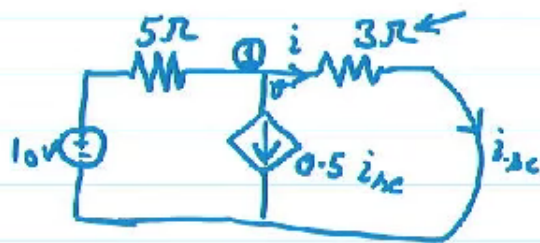

$$\frac{v - 10}{5} + 0.5 i_{sc} + i_{sc} = 0$$


$$v = 3 \cdot i_{sc}$$

$$\frac{3 i_{sc} - 10}{5} + 1.5 i_{sc} = 0$$

$$i_{sc} = 0.95 \text{ Amp.}$$

$$R_{int} = \frac{V_{oc}}{I_{sc}} = \frac{10}{0.95}$$

$$R_{int} = 10.52 \Omega$$

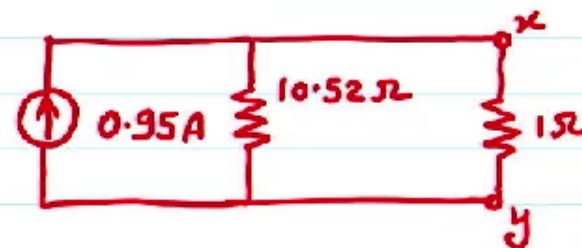

Maximum Power Transfer Theorem :

Maximum Power is transferred to the load when the load resistance equals to the Thevenin's resistance as seen from the load.

